


Labs/01-gates

De Morgan's Laws

Function Table

| c | b | a | f(c,b,a) |
|---|---|---|----------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

Picture

 

Code

```
-----  
--  
-- Example of basic OR, AND, XOR gates.  
-- Nexys A7-50T, Vivado v2020.1, EDA Playground  
--  
-- Copyright (c) 2019-2020 Tomas Fryza  
-- Dept. of Radio Electronics, Brno University of Technology, Czechia  
-- This work is licensed under the terms of the MIT license.  
--  
-----  
  
library ieee;                -- Standard library  
use ieee.std_logic_1164.all;-- Package for data types and logic operations
```

```

-----
-- Entity declaration for basic gates
-----

entity gates is
  port(
    a_i    : in  std_logic;      -- Data input
    b_i    : in  std_logic;      -- Data input
    c_i    : in  std_logic;      -- Data input
    f_o    : out std_logic;      -- OR output function
    fna_o  : out std_logic;      -- NAND output function
    fno_o  : out std_logic;      -- NOR output function
    --for_o : out std_logic;      -- OR output function
    --fand_o : out std_logic;     -- AND output function
    --fxor_o : out std_logic;     -- XOR output function
  );
end entity gates;

-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
  f_o    <= ((not b_i) and a_i) or ((not c_i) and (not b_i));
  fna_o  <= ((b_i nand b_i) nand a_i) nand ((c_i nand c_i) nand (b_i nand b_i));
  fno_o  <= (((a_i nor a_i) nor b_i) nor (b_i nor c_i)) nor (((a_i nor a_i) nor
b_i) nor (b_i nor c_i));
  --for_o <= a_i or b_i;
  --fand_o <= a_i and b_i;
  --fxor_o <= a_i xor b_i;

end architecture dataflow;

```

Link

[EDA Plauground](#)

Distributive Functions

Code

```

-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

```

```

-----
-- Entity declaration for basic gates
-----

```

```
entity gates is
  port(
    x_i      : in  std_logic;      -- Data input
    y_i      : in  std_logic;      -- Data input
    z_i      : in  std_logic;      -- Data input

    one_o     : out std_logic;      -- First postulate
    two_o     : out std_logic;      -- Second postulate
    three_o    : out std_logic;     -- Third postulate
    four_o    : out std_logic;     -- Fourth postulate

    l1l_o     : out std_logic;      -- Left part of the first law equation
    l1r_o     : out std_logic;      -- Right part of the first law equation
    l2l_o     : out std_logic;      -- Left part of the second law equation
    l2r_o     : out std_logic;      -- Right part of the second law equation
  );
end entity gates;


-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
  one_o  <= x_i and not(x_i);
  two_o  <= x_i or not(x_i);
  three_o <= x_i or x_i or x_i;
  four_o <= x_i and x_i and x_i;

  l1l_o  <= (x_i and y_i) or (x_i and z_i);
  l1r_o  <= x_i and (y_i or z_i);
  l2l_o  <= (x_i or y_i) and (x_i or z_i);
  l2r_o  <= x_i or (y_i and z_i);

end architecture dataflow;
```

Picture

 

Link

[EDA Plauground](#)