

Labs/04-labs

GitHub Link

[GitHub - Daniel Havránek \(Dan5049\)](#)

1. Preparation tasks

Buttons

Button	FPGA pin	FPGA package pin
BTNL	IO_L12P_T1_MRCC_14	P17
BTNR	IO_L10N_T1_D15_14	M17
BTNU	IO_L4N_T0_D05_14	M18
BTND	IO_L9N_T1_DQS_D13_14	P18
BTNC	IO_L9P_T1_DQS_14	N17

Time interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
2 ms	200 000	x"3_0d40"	b"0011_0000_1101_0100_0000"
4 ms	400 000	x"6_1a80"	b"0110_0001_1010_1000_0000"
10 ms	1 000 000	x"f_4240"	b"1111_0100_0010_0100_0000"
250 ms	25 000 000	x"17d_7840"	b"0001_0111_1101_0111_1000_0100_0000"
500 ms	50 000 000	x"2fa_f080"	b"0010_1111_1010_1111_0000_1000_0000"
1 sec	100 000 000	x"5f5_e100"	b"0101_1111_0101_1110_0001_0000_0000"

Bidirectional counter

Code of the process `p_cnt_up_down`

```
architecture behavioral of cnt_up_down is

    -- Local counter
    signal s_cnt_local : unsigned(g_CNT_WIDTH - 1 downto 0);

begin
    -----
```

```

-- p_cnt_up_down:
-- Clocked process with synchronous reset which implements n-bit
-- up/down counter.
-----
p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then                -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then              -- Test if counter is enabled

            -- TEST COUNTER DIRECTION HERE

            if (cnt_up_i = '1') then
                s_cnt_local <= s_cnt_local + 1;
            else
                s_cnt_local <= s_cnt_local - 1;
            end if;

        end if;
    end if;
end process p_cnt_up_down;

-- Output must be retyped from "unsigned" to "std_logic_vector"
cnt_o <= std_logic_vector(s_cnt_local);

end architecture behavioral;

```

Reset and stimulus process from testbench

```

p_reset_gen : process
begin
    s_reset <= '0';
    wait for 12 ns;

    -- Reset activated
    s_reset <= '1';
    wait for 25 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----
-- Data generation process

```

```

-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;

    -- Enable counting
    s_en      <= '1';


    -- Change counter direction
    s_cnt_up <= '1';
    wait for 380 ns;
    s_cnt_up <= '0';
    wait for 220 ns;


    -- Disable counting
    s_en      <= '0';

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```

Simulated waveforms

 

 

Top level

Code from source file

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity top is
    Port (
        CLK100MHz    : in STD_LOGIC;
        BTNC         : in STD_LOGIC;
        SW           : in STD_LOGIC_VECTOR (1 - 1 downto 0);
        LED          : out STD_LOGIC_VECTOR (4 - 1 downto 0);
        CA           : out STD_LOGIC;
        CB           : out STD_LOGIC;
        CC           : out STD_LOGIC;
        CD           : out STD_LOGIC;
        CE           : out STD_LOGIC;
        CF           : out STD_LOGIC;
        CG           : out STD_LOGIC;
        AN           : out STD_LOGIC_VECTOR (8 - 1 downto 0));
end top;

-----
-- Architecture body for top level
```

```
-----
architecture Behavioral of top is
```

```
-- Internal clock enable
signal s_en : std_logic;
-- Internal counter
signal s_cnt : std_logic_vector(4 - 1 downto 0);
```

```
begin
```

```
-----
-- Instance (copy) of clock_enable entity
```

```
clk_en0 : entity work.clock_enable
  generic map(
    --- WRITE YOUR CODE HERE
    g_MAX => 100000000
  )
  port map(
    --- WRITE YOUR CODE HERE
    clk      => CLK100MHz,
    reset    => BTNC,
    ce_o     => s_en
  );
```

```
-----
-- Instance (copy) of cnt_up_down entity
```

```
bin_cnt0 : entity work.cnt_up_down
  generic map(
    --- WRITE YOUR CODE HERE
    g_CNT_WIDTH => 4
  )
  port map(
    --- WRITE YOUR CODE HERE
    clk      => CLK100MHz,
    reset    => BTNC,
    en_i     => s_en,
    cnt_up_i => SW(0),
    cnt_o    => s_cnt
  );
```

```
-- Display input value on LEDs
```

```
LED(3 downto 0) <= s_cnt;
```

```
-----
-- Instance (copy) of hex_7seg entity
```

```
hex2seg : entity work.hex_7seg
  port map(
    hex_i    => s_cnt,
    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
```

```
        seg_o(0) => CG
    );

    -- Connect one common anode to 3.3V
    AN <= b"1111_1110";

end architecture Behavioral;
```

Image of the top layer with 4-bit and 16-bit counter

At the top of the picture, there is 4-bit bidirectional counter connected to 7-segment display. Below the 4-bit counter, there is 16-bit bidirectional counter with different time domain. Output of this 16-bit counter is not connected.

