

# Labs/01-gates

## GitHub Link


[GitHub - Daniel Havránek \(Dan5049\)](#)

## De Morgan's Laws

### Function Table

c	b	a	f(c,b,a)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

## Picture

 

## Code

```
-----
--
-- Example of basic OR, AND, XOR gates.
-- Nexys A7-50T, Vivado v2020.1, EDA Playground
--
-- Copyright (c) 2019-2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
```

```

--
-----

library ieee;           -- Standard library
use ieee.std_logic_1164.all; -- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----

entity gates is
    port(
        a_i    : in  std_logic;    -- Data input
        b_i    : in  std_logic;    -- Data input
        c_i    : in  std_logic;    -- Data input
        f_o    : out std_logic;    -- OR output function
        fna_o  : out std_logic;    -- NAND output function
        fno_o  : out std_logic;    -- NOR output function
        --for_o : out std_logic;    -- OR output function
        --fand_o : out std_logic;    -- AND output function
        --fxor_o : out std_logic;    -- XOR output function
    );
end entity gates;

-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
    f_o    <= ((not b_i) and a_i) or ((not c_i) and (not b_i));
    fna_o  <= ((b_i nand b_i) nand a_i) nand ((c_i nand c_i) nand (b_i nand b_i));
    fno_o  <= (((a_i nor a_i) nor b_i) nor (b_i nor c_i)) nor (((a_i nor a_i) nor
b_i) nor (b_i nor c_i));
    --for_o <= a_i or b_i;
    --fand_o <= a_i and b_i;
    --fxor_o <= a_i xor b_i;

end architecture dataflow;

```

Link

[EDA Plauground](#)

## Distributive Functions

Code

```

-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

-----
-- Entity declaration for basic gates
-----

entity gates is
    port(
        x_i      : in  std_logic;      -- Data input
        y_i      : in  std_logic;      -- Data input
        z_i      : in  std_logic;      -- Data input

        one_o    : out std_logic;      -- First postulate
        two_o    : out std_logic;      -- Second postulate
        three_o   : out std_logic;      -- Third postulate
        four_o    : out std_logic;      -- Fourth postulate

        l1l_o    : out std_logic;      -- Left part of the first law equation
        l1r_o    : out std_logic;      -- Right part of the first law equation
        l2l_o    : out std_logic;      -- Left part of the second law equation
        l2r_o    : out std_logic;      -- Right part of the second law equation
    );
end entity gates;

-----
-- Architecture body for basic gates
-----


architecture dataflow of gates is
begin
    one_o    <= x_i and not(x_i);
    two_o    <= x_i or not(x_i);
    three_o  <= x_i or x_i or x_i;
    four_o   <= x_i and x_i and x_i;

    l1l_o    <= (x_i and y_i) or (x_i and z_i);
    l1r_o    <= x_i and (y_i or z_i);
    l2l_o    <= (x_i or y_i) and (x_i or z_i);
    l2r_o    <= x_i or (y_i and z_i);

end architecture dataflow;

```

Picture

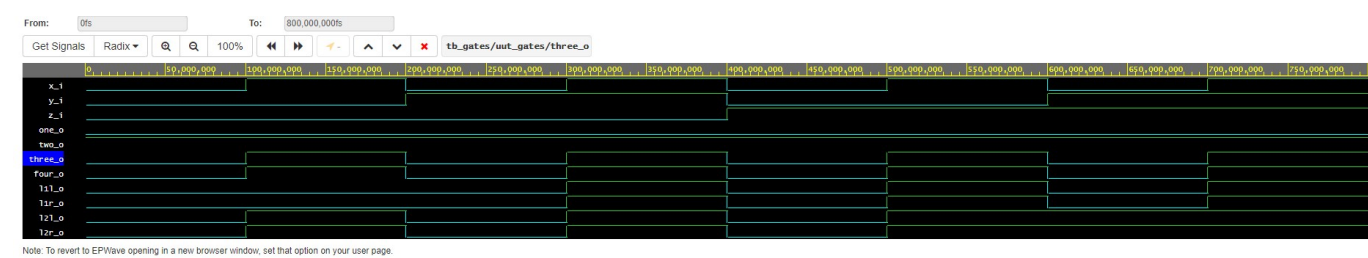

Link

[EDA Plauground](#)